


Digital Logic Circuits 'Circuit Diagrams' ELEC2200 Summer 2009

David J. Broderick
brodedj@auburn.edu
<http://www.auburn.edu/~brodedj>
Office: Broun 360



Circuit Diagrams

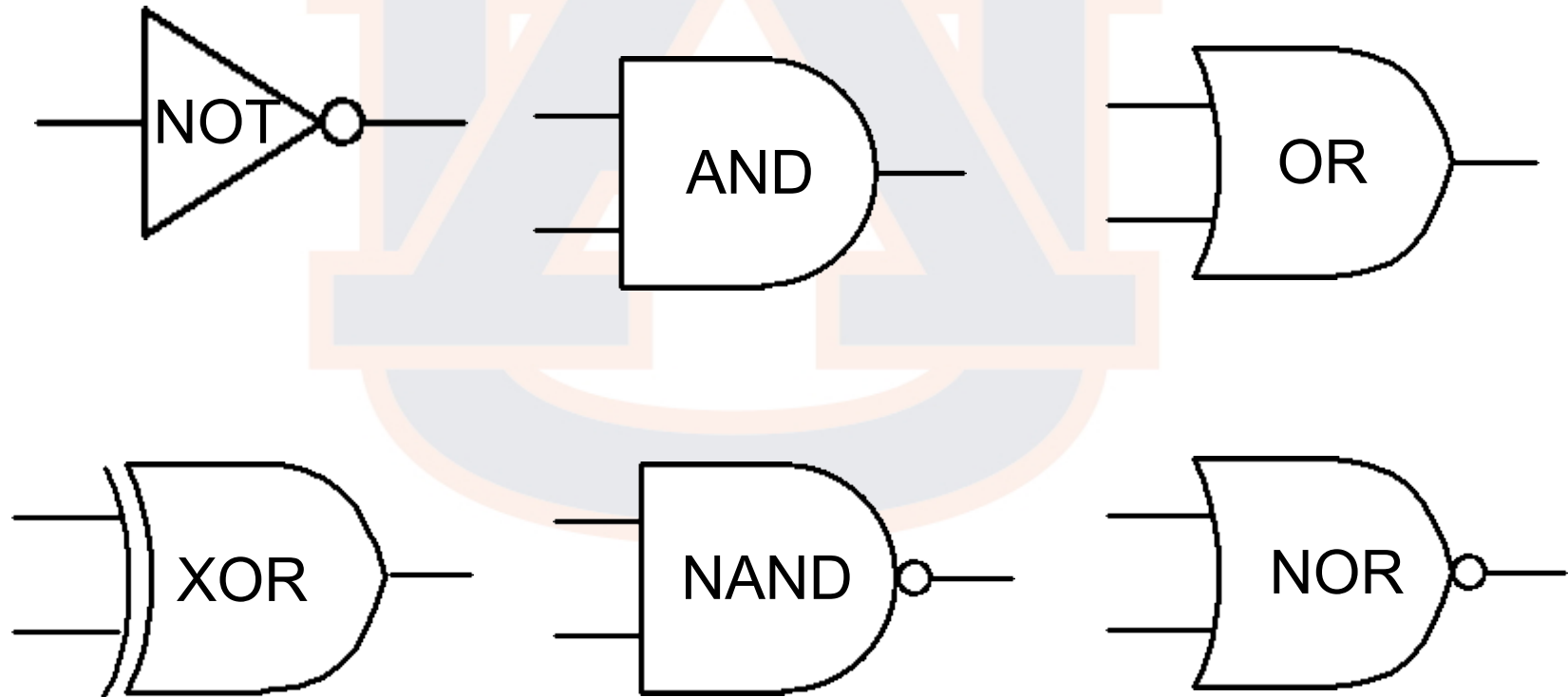
- Let's employ our design techniques and draw the corresponding circuit




Elementary Gates

- Complement, Invert, Not
- Two notations: A' and \bar{A}
- And
- Notated as $A \cdot B$

A	\bar{A}
0	1
1	0

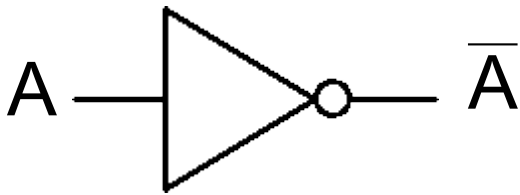


A	B	$A \cdot B$
0	0	0
0	1	0
1	0	0
1	1	1

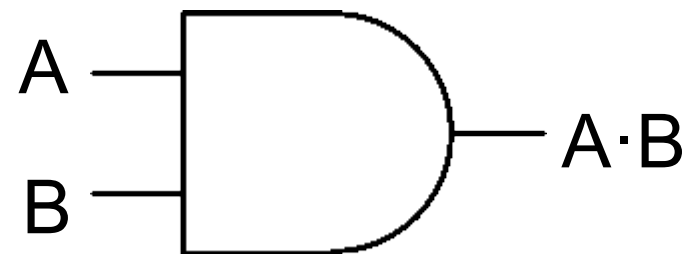

Elementary Gates

- Or
- Notated as $A+B$


A	B	$A+B$
0	0	0
0	1	1
1	0	1
1	1	1

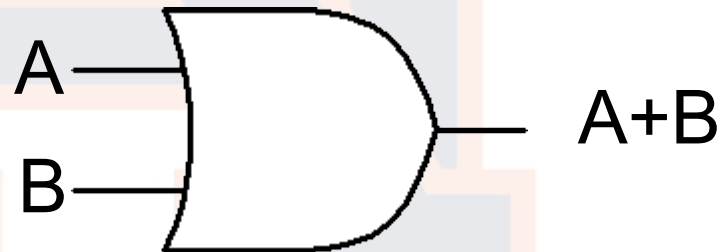

Elementary Gates


- NAND

- $\overline{A \cdot B}$

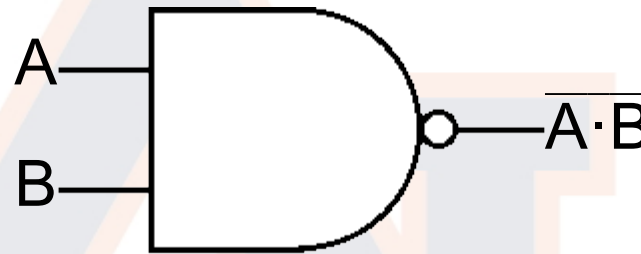

- DeMorgan's gives us $\overline{A \cdot B} = \overline{A} + \overline{B}$


A	B	$\overline{A \cdot B}$
0	0	1
0	1	1
1	0	1
1	1	0

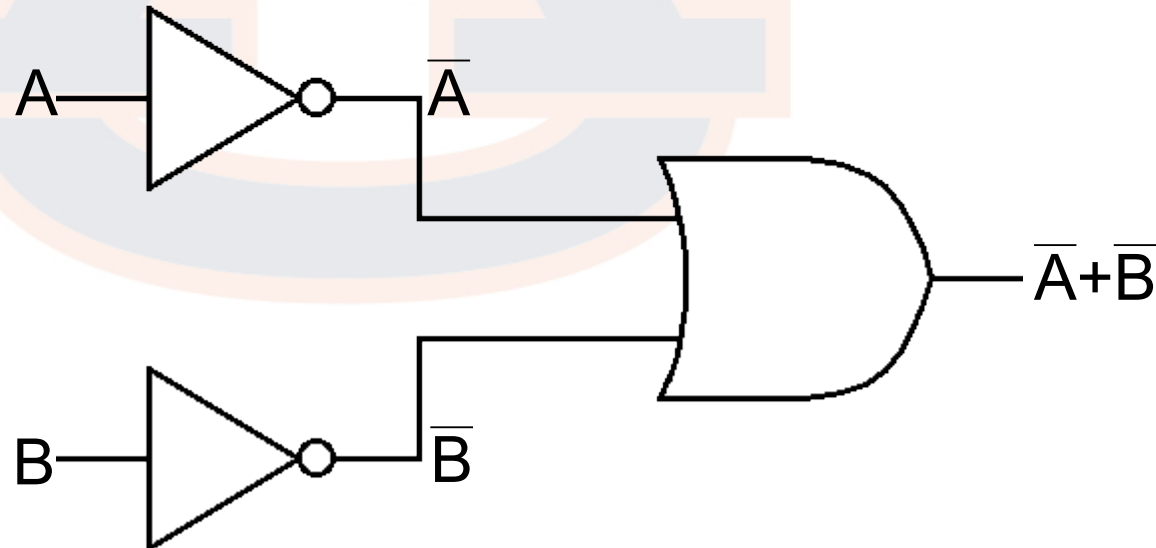

Elementary Gates


- NOR

- $\overline{A+B}$

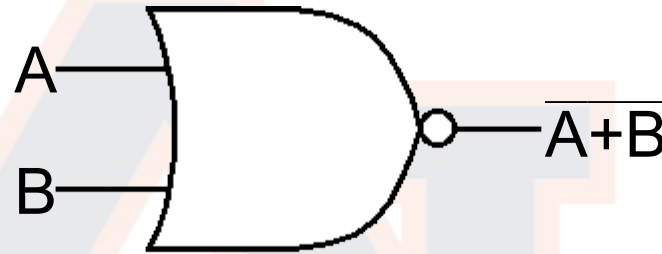


- DeMorgan's gives us $\overline{A+B} = \overline{A} \cdot \overline{B}$

A	B	$\overline{A+B}$
0	0	1
0	1	0
1	0	0
1	1	0

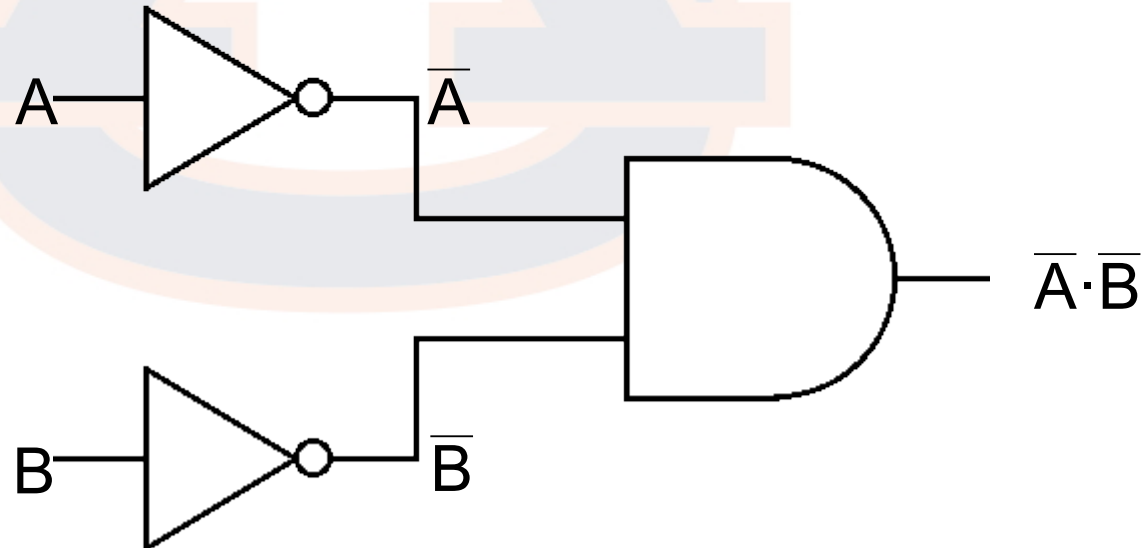


Elementary Gates

- XOR

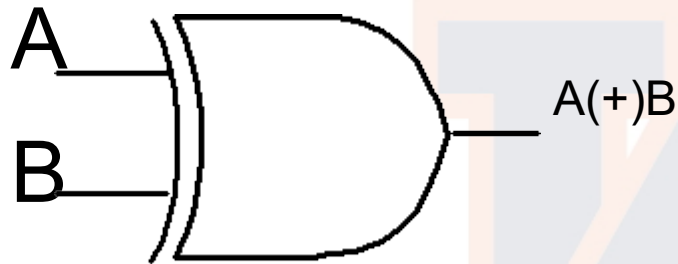

A	B	$A(+)B$
0	0	0
0	1	1
1	0	1
1	1	0

- XNOR

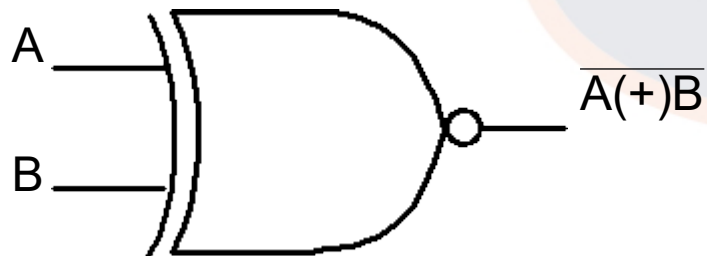

A	B	$\overline{A(+)B}$
0	0	1
0	1	0
1	0	0
1	1	1




XOR Properties

- XOR has some unique properties
 - Controlled Inverter
 - $A(+)0=A$
 - $A(+)1=\bar{A}$
 - Invert one XOR input \rightarrow XNOR
 - $A(+)\bar{B}=\bar{A}(+)B=\overline{A(+)B}$
 - Invert one XOR input \rightarrow XNOR
 - $(A(+)\bar{B})'=(\bar{A}(+)B)'=A(+)B$
 - Constant output
 - $A(+)A=0$
 - $A(+)\bar{A}=1$
- Multiple implementations of XOR possible



XOR Implementations

- 4 Gates

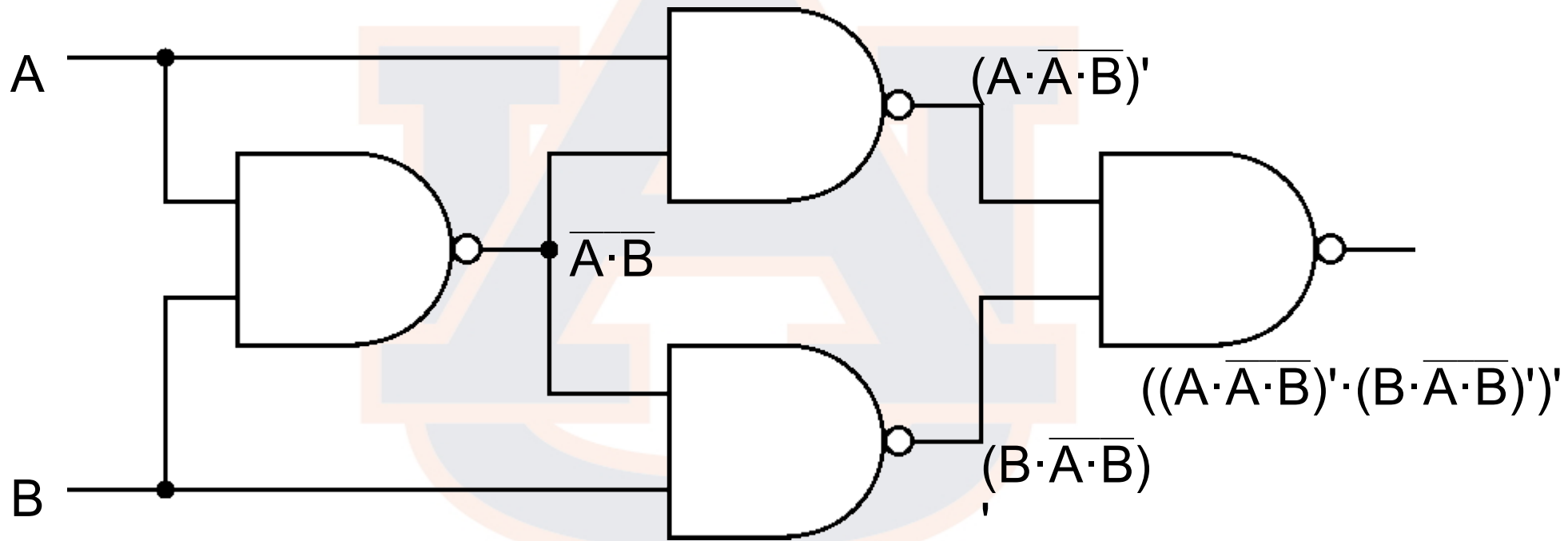


$$((A \cdot \overline{A} \cdot B)' \cdot (B \cdot \overline{A} \cdot B)')' = A(+)B$$



XOR Implementations

- 5 Gates

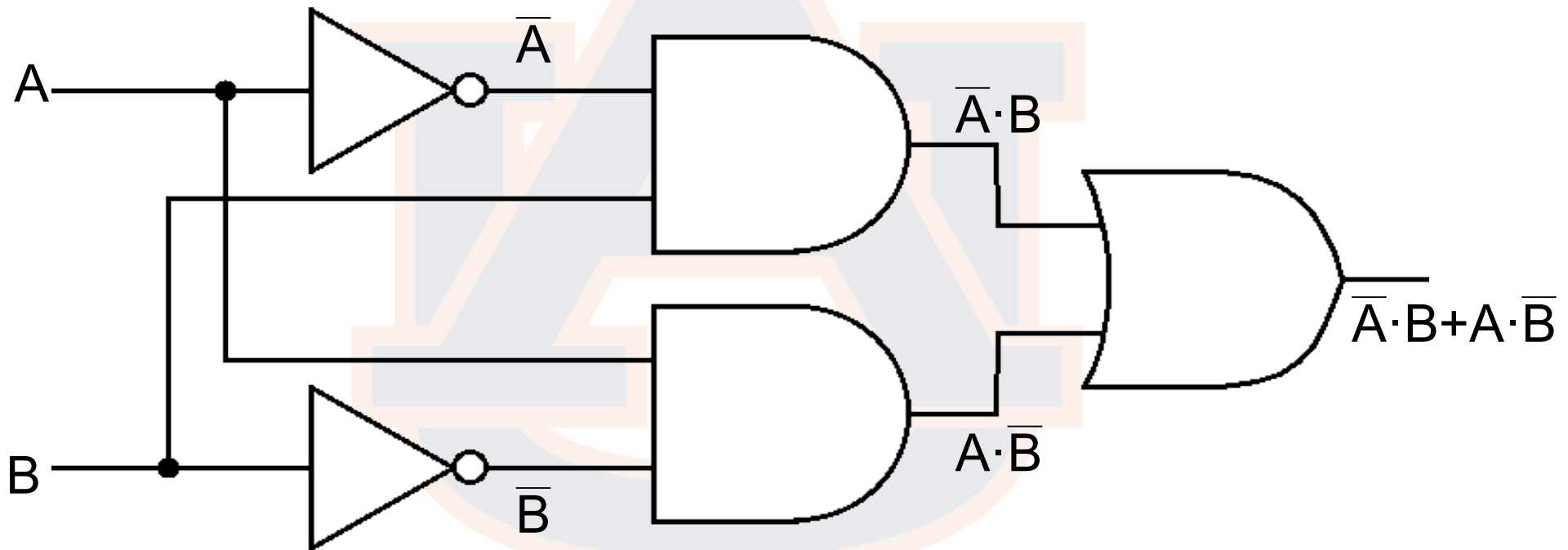


$$\bar{A} \cdot B + A \cdot \bar{B} = A(+)B$$



XOR Implementations

- 3 Gates

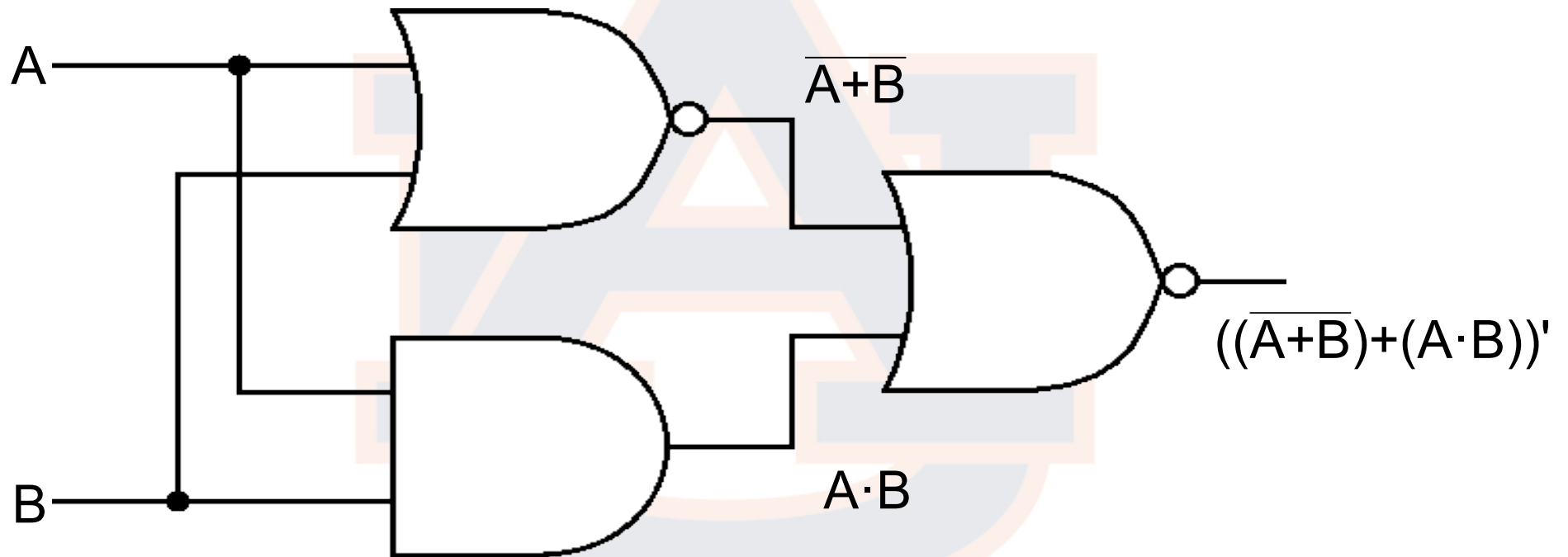


$$((\overline{A+B}) + (A \cdot B))' = A(+)B$$



SOP/POS Circuits


- SOP expressions

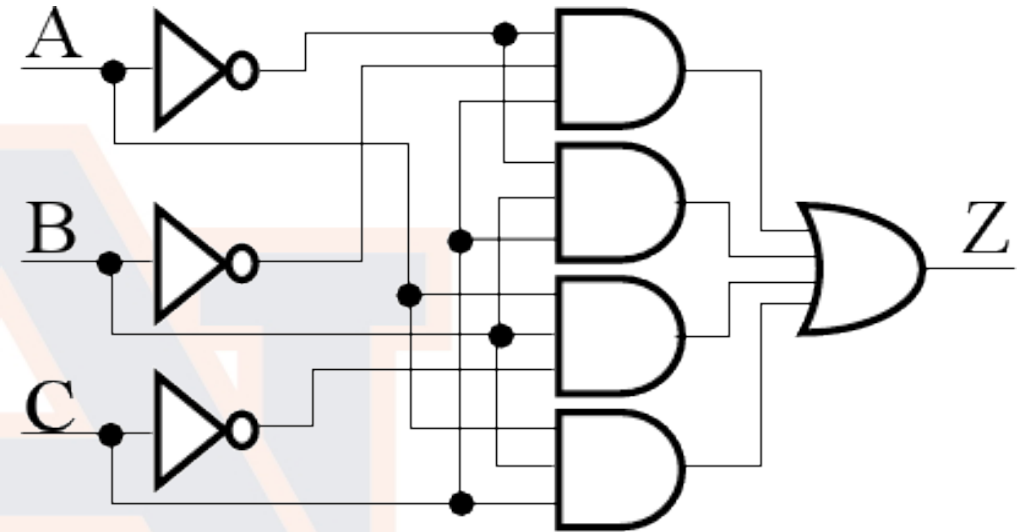- AND-OR
- Inverters for complemented literals
- $Z = \bar{A} \cdot \bar{B} \cdot C + \bar{A} \cdot B \cdot C + A \cdot B \cdot \bar{C} + A \cdot B \cdot C$
- 2-level AND-OR logic




- POS expressions

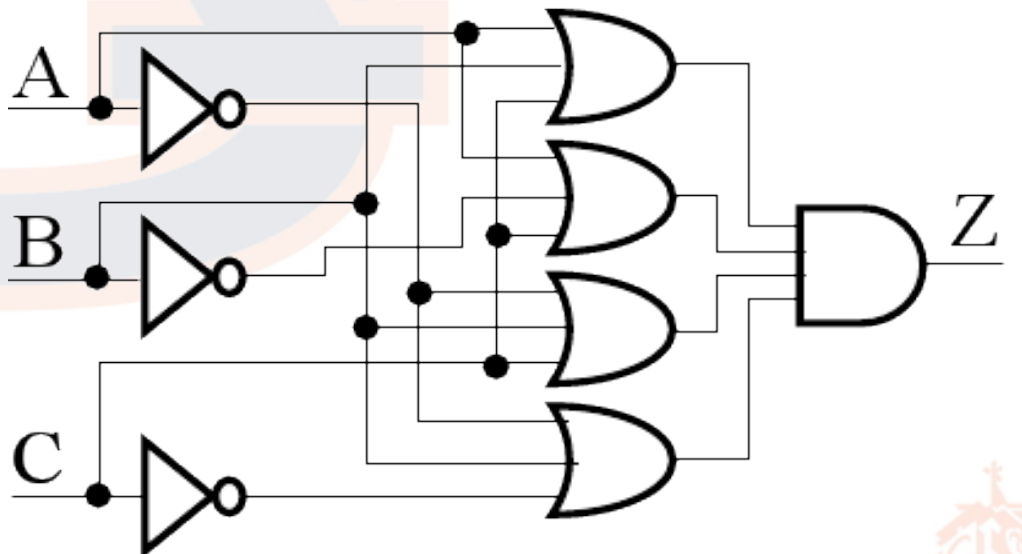- OR-AND
- Inverters for complemented literals
- $Z = (A+B+C) \cdot (A+\bar{B}+C) \cdot (\bar{A}+B+C) \cdot (\bar{A}+B+\bar{C})$
- 2-level OR-AND logic




Gate Level Representation

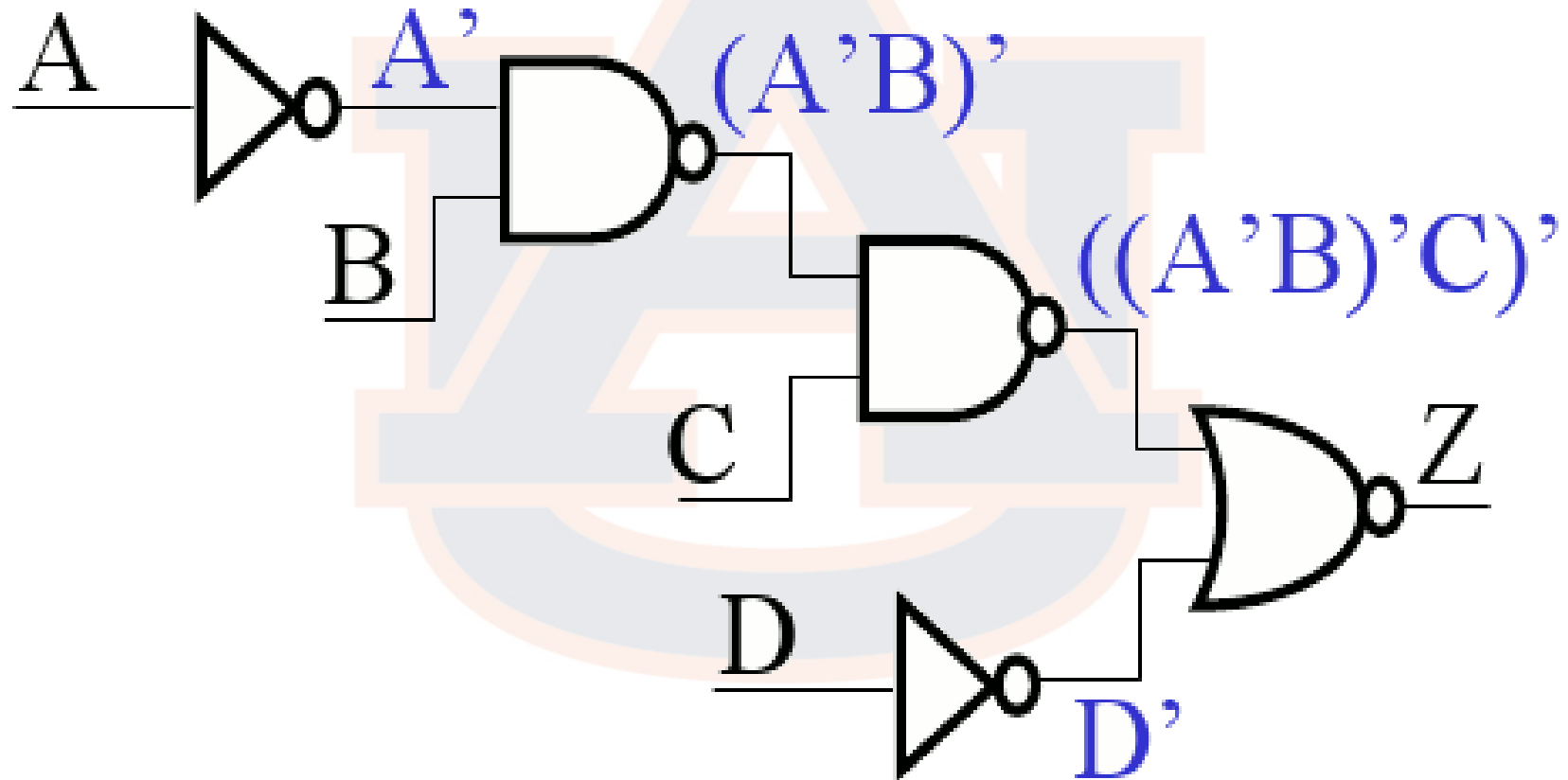- From $Z = \overline{(((A' \cdot B)' \cdot C)' + D')}$



Circuit Analysis

- Recovering truth table from design

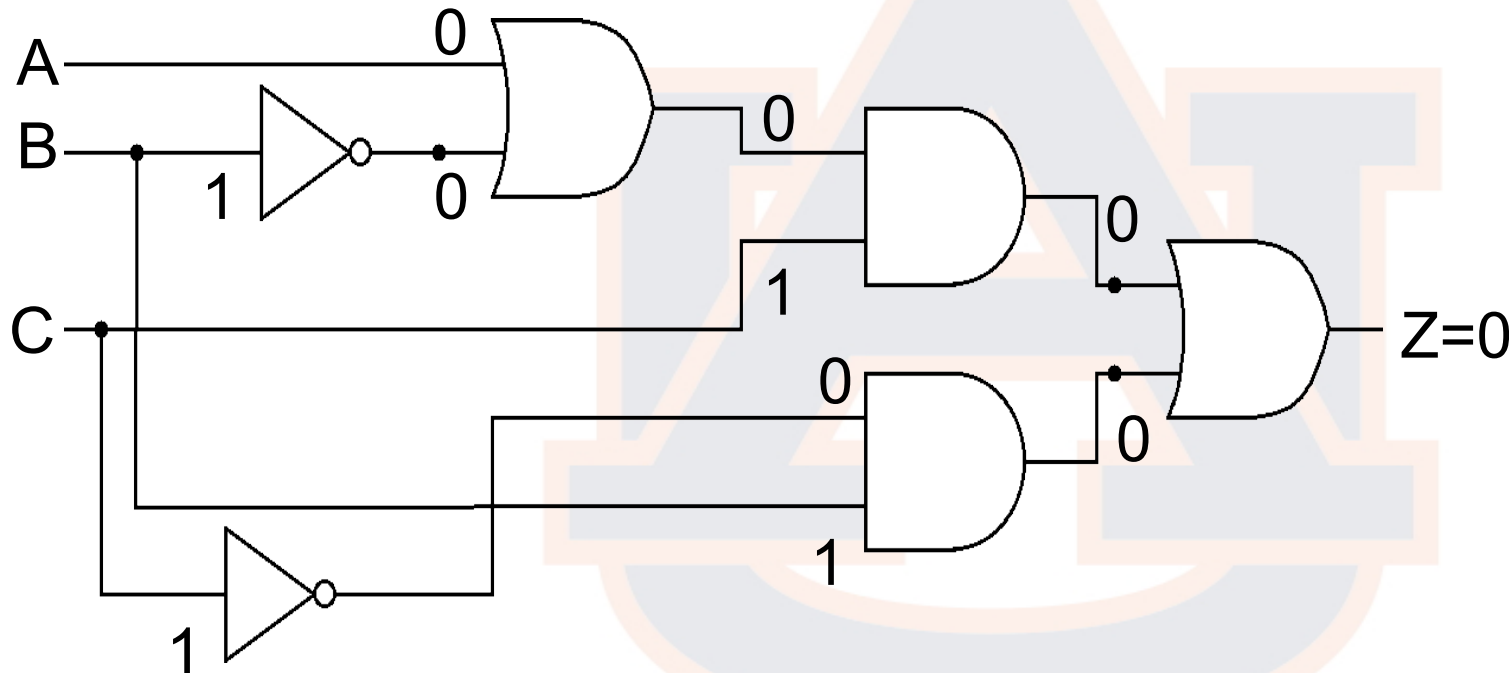


A	B	C	Z
0	0	0	
0	0	1	
0	1	0	
0	1	1	0
1	0	0	
1	0	1	
1	1	0	
1	1	1	

- Apply inputs for each row and calculate output



Circuit Analysis

- Recovering the expression

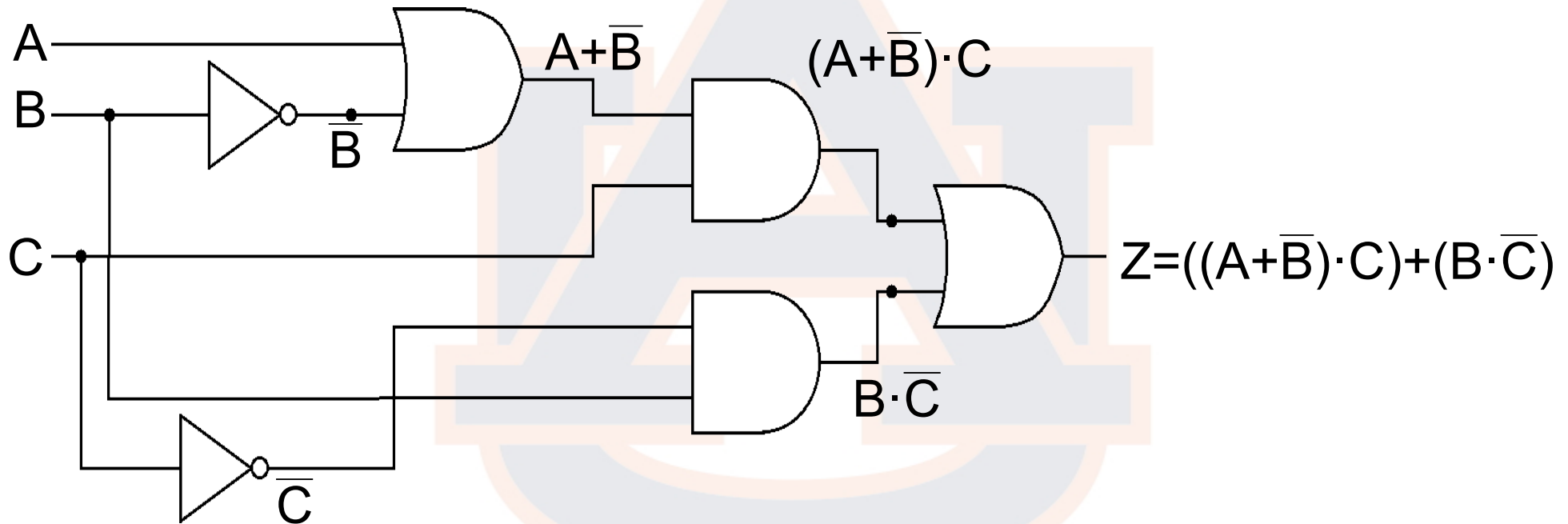


- Propagate the expressions from input to output



Circuit Analysis

- Find the expression and truth table



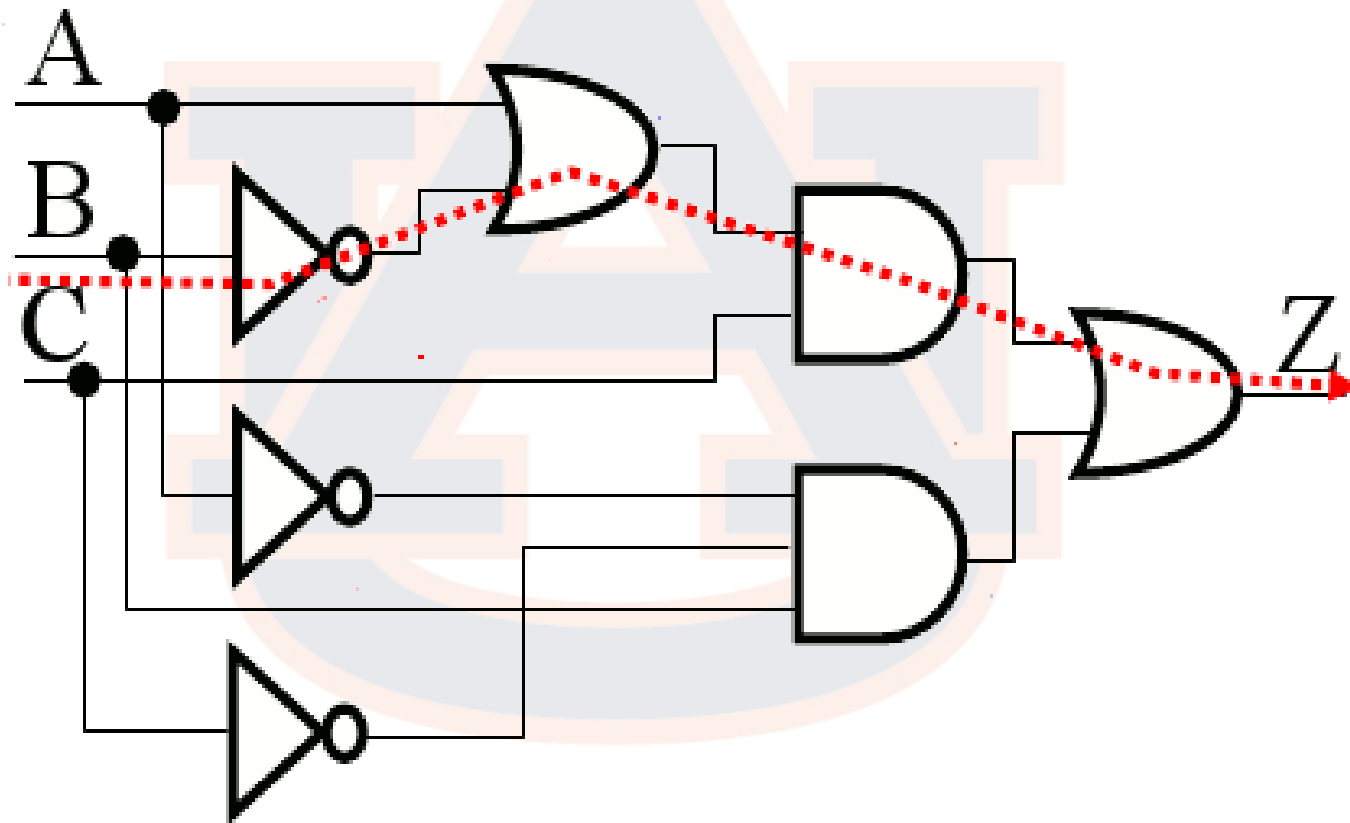


Functionally Complete Sets

- If any digital circuit can be built from a set of gates (types), that set is said to be functionally complete
 - NOT, AND, OR
 - NAND
 - NOR
 - Multiplexers
- If a set can be used to construct NOT, AND, and OR functions it is functionally complete



NAND Logic

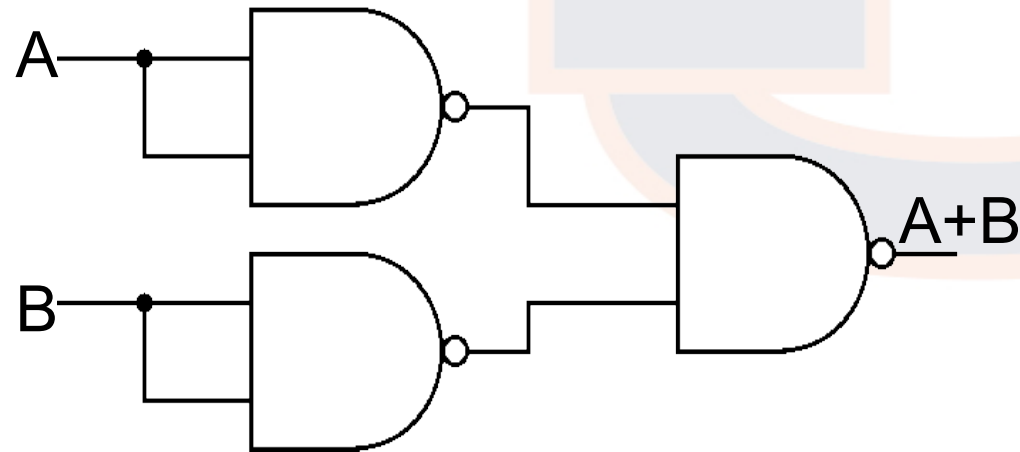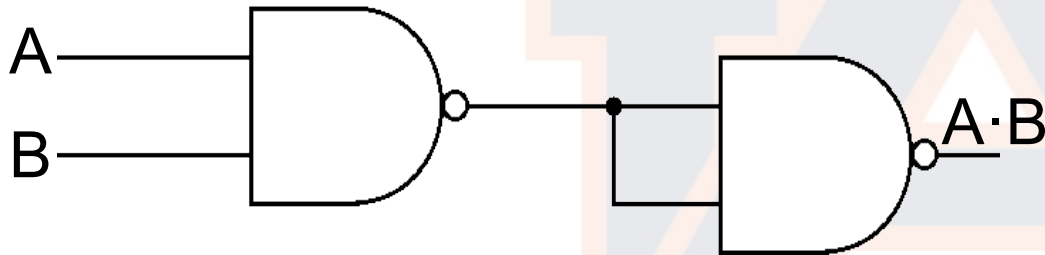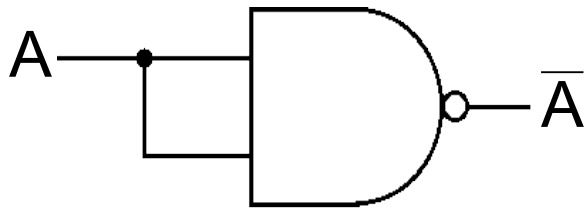

- The NAND gate is a functionally complete set
- DeMorgan's needed for OR function
- Same approach can be taken with NOR
- Can build any circuit from NAND gates alone

